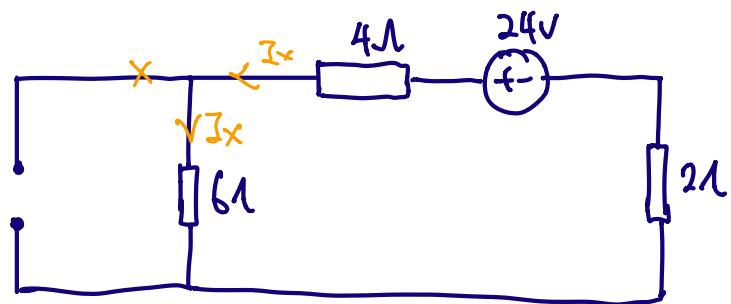


Omit 24V supply

$$I_x' = \frac{4+2}{6+4+2} (5) \\ = 2.5A (\downarrow)$$




Omit 5A source

$$I_x'' = \frac{24}{6+4+2} = 2A (\downarrow)$$

$$\therefore I_x = I_x' + I_x'' \\ = 2.5 + 2 \\ = 4.5A$$

$$\text{Power dissipate} = I_x^2 (R) \\ = (4.5)^2 (6) \\ = 121.5 W$$

(absorb)

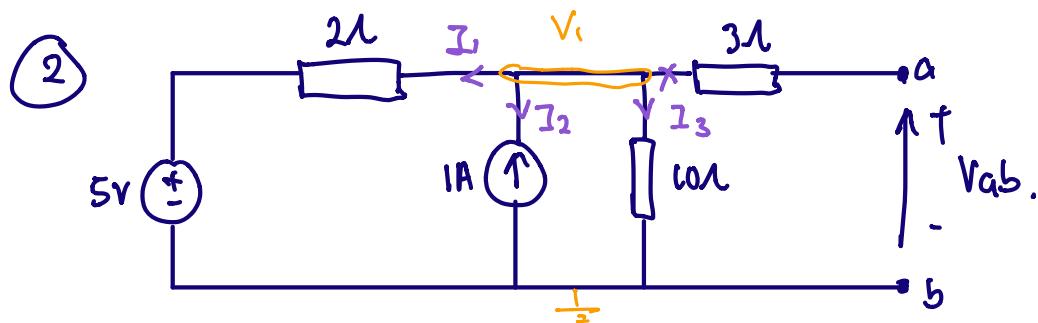


By KCL:

$$\frac{V_1 - 5}{2} - 1 + \frac{V_1}{10} = 0$$

$$(10) \quad 5V_1 - 25 - 10 + V_1 = 0 \quad V_1 = V_{ab} = 5.83V$$

$$6V_1 = 35$$

$$V_1 = 5.83V$$

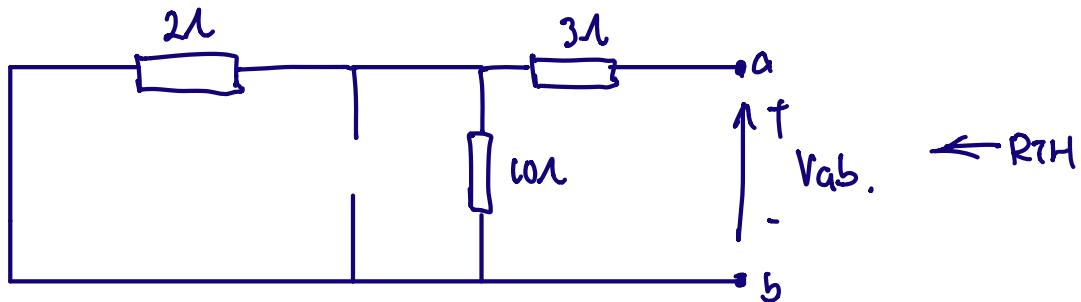


$$R_{TH} = 2\Omega // 10\mu F + 3\Omega$$

$$= \left(\frac{1}{2} + \frac{1}{10} \right)^{-1} + 3$$

$$= 4.67\Omega$$

Thevenin circuit:

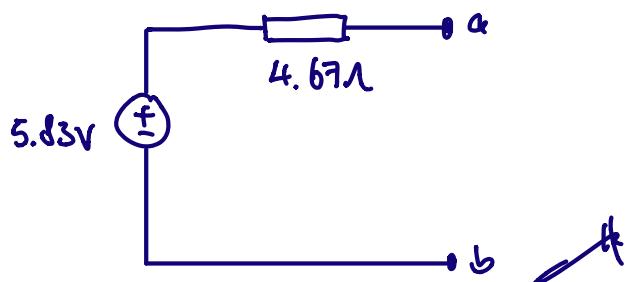

(3)

$$Z_L = j\omega L$$

$$= j2\pi(50)(6.5 \times 10^{-3})$$

$$= j2.042$$

$$Z_1 = 2 + j2.042$$

$$Z_C = \frac{1}{j\omega C}$$

$$= \frac{1}{j(2\pi)(50)1.06 \times 10^{-3}} \text{ (xj)} \text{ (xj)}$$

$$= \frac{-j}{2\pi(50)1.06 \times 10^{-3}}$$

$$= -j3$$

$$Z_2 = 1-j3$$


$$Z_{\text{total}} = Z_1 // Z_2$$

$$= \left(\frac{1}{2+j2.042} + \frac{1}{1-j3} \right)^{-1}$$

$$= 2.84 - j0.412$$

$$= 2.87 \angle \underline{-8.26^\circ} \text{ } \cancel{\text{A}}$$

(4)

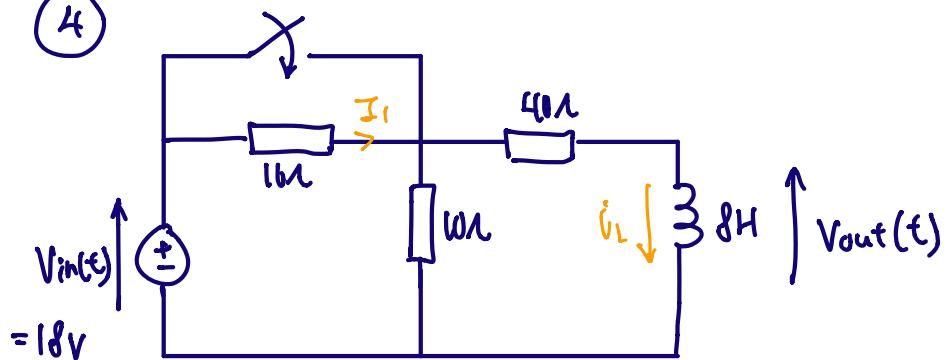

a) at $t=0$, current in inductor cannot change instantaneously.


$$i_L(0^-) = i_L(0^+)$$

$$10\Omega \parallel 40\Omega = \left(\frac{1}{10} + \frac{1}{40}\right)^{-1} \Rightarrow 8\Omega$$

$$V = \frac{8}{16+8} (18) = 6V$$


$$i_L(0^+) = \frac{6}{40} = 0.15A$$

at $t=\infty$

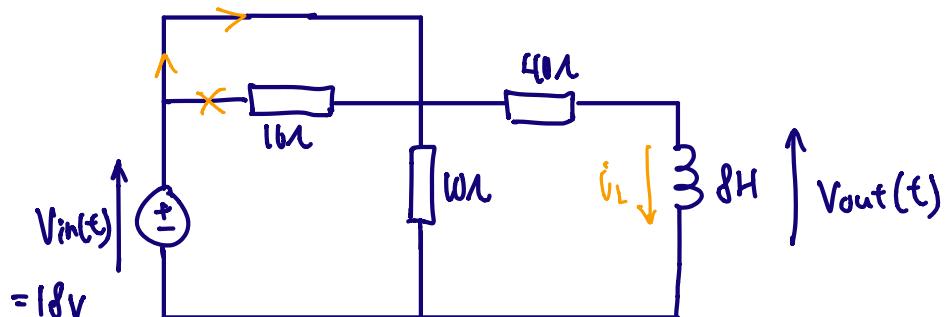

$$i_L = \frac{18}{40} = 0.45A$$

4b)

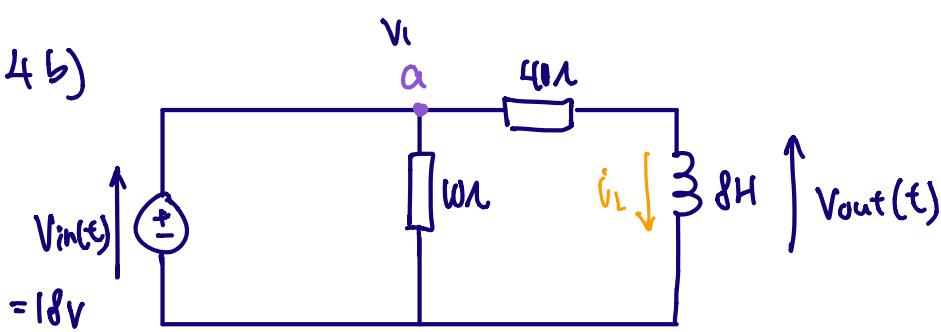

$$V_{in}(t) = 40 I_L(t) + V_{out}(t)$$

$$\text{using } V_{out}(t) = L \frac{dI_L}{dt},$$

$$V_{in}(t) = 40 I_L(t) + L \frac{dI_L}{dt}$$

$$V_{in}(t) = 40 I_L(t) + 8 \frac{dI_L}{dt}$$

$$(i) \quad \frac{V_{in}(t)}{8} = 5 I_L(t) + \frac{dI_L}{dt}$$

$$5 I_L(t) + \frac{dI_L}{dt} = \frac{V_{in}(t)}{8} \quad (\text{shown})$$

c) By using general approach:

$$\tau = \frac{L}{R}, \quad R = 4\Omega, \quad L = 8$$

$$i_L \text{ initial} = 0.15A$$

$$\tau = \frac{8}{40} = \frac{1}{5}$$


$$i_L \text{ final} = 0.45A$$

$$I_L = I_f - (I_i - I_f) e^{-\frac{t}{\tau}}$$

$$= 0.45 - (0.15 - 0.45) e^{-5t}$$

$$= 0.45 + 0.3 e^{-5t} \quad \text{for } t \geq 0$$

5

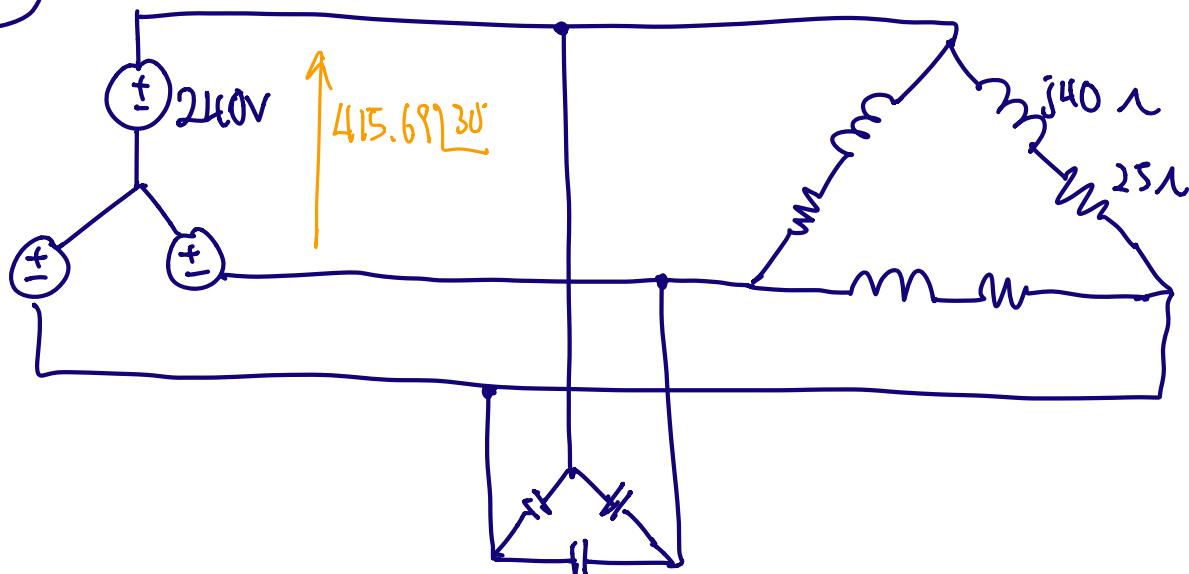

a) $V_L = \sqrt{3} V_{ph} \angle 30^\circ$ For delta $V_L = V_{ph} = 415.69 \angle 30^\circ \text{ V}$

$$= \sqrt{3} (240) \angle 30^\circ$$

$$= 415.69 \angle 30^\circ \text{ V}$$

#

b) $I_{ph} = \frac{415.69 \angle 30^\circ}{25+j40}$

$$= 7.781 - j4.1365$$

$$= 8.813 \angle -28^\circ \text{ A}$$

c) $I_L = \sqrt{3} I_{ph} \angle -30^\circ$

$$= \sqrt{3} (8.813) \angle -28 - 30^\circ$$

$$= 15.26 \angle -58^\circ \text{ A}$$

d) $\text{P}^* = \sqrt{3} V_L I_L^*$

$$= \sqrt{3} (415.69 \angle 30^\circ \times 15.26 \angle 58^\circ)$$

$$= 10987.142 \angle 88^\circ$$


$$= 383.45 + j 10980.45$$

$P = 383.45 \text{W}$

e) new pf = 0.95 old Q = 88

$$\cos \theta = 0.95$$

$$\theta = 18.19^\circ$$

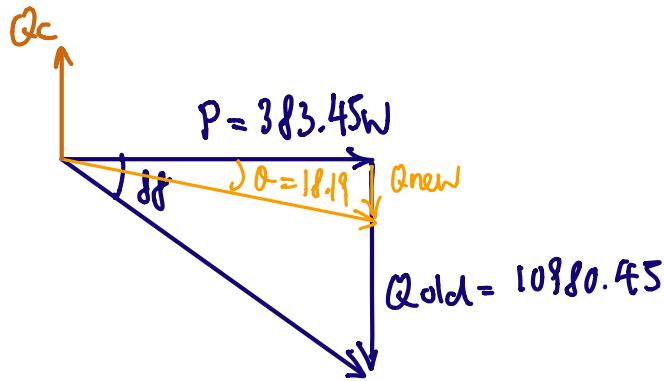

$$Q_C = Q_{\text{old}} - Q_{\text{new}}$$

$$= 10980.45 - 126$$

$$= 10854.45 \text{ VA}_r$$

$$Q_C \text{ per phase} = \frac{10854.45}{3}$$

$$= 3618.15 \text{ VA}_r$$

$$\tan(18.19) = \frac{Q_{\text{new}}}{383.45}$$

$$Q_{\text{new}} = 126 \text{ VA}_r$$

$$Q_C = \frac{(415.69)^2}{X_C}$$

$$3618.15 = \frac{172798.176}{\frac{1}{wC}}$$

$$3618.15 = \frac{172798.176}{\frac{1}{2\pi(50)(C)}}$$

$$C = 66.6 \mu F$$

(c)

a) 4kVA, $\frac{V_1}{V_2} = \frac{200}{400} = \frac{1}{2} = 9$


open circuit test

$$P = VI \cos\theta$$

$$65 = 200(0.6) \cos\theta$$

$$\cos\theta = 0.5417$$

$$\theta = 57.2^\circ$$

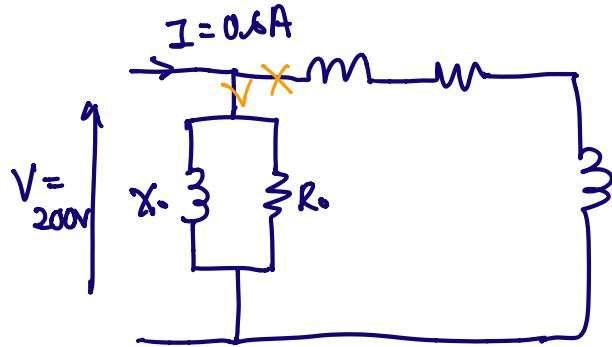

$$\begin{aligned} R_o &= \frac{200}{0.6 \cos\theta} \\ &= \frac{200}{0.6(0.5417)} \\ &= 615.35 \Omega \end{aligned}$$


$$\begin{aligned} X_o &= \frac{200}{0.6 \sin\theta} \\ &= \frac{200}{0.6 \sin(57.2)} \\ &= 396.56 \Omega \end{aligned}$$

short circuit test

$$80 = 18(7) \cos\theta$$

$$\cos\theta = 0.6349$$


$$\theta = 50.586^\circ$$

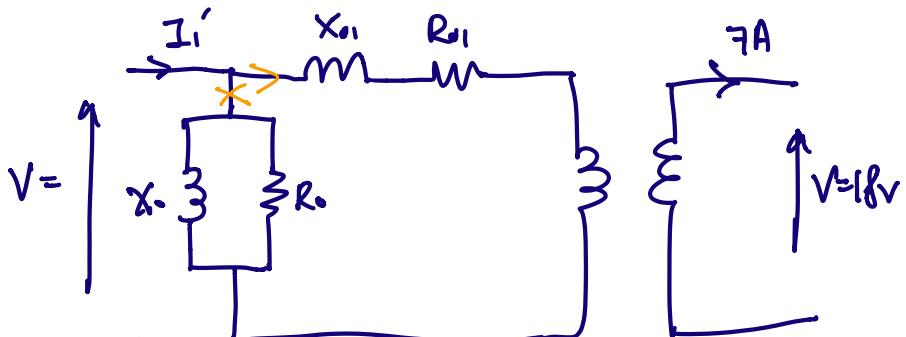

$$P = I_2^2 R_{o2}$$

$$80 = 7^2 (R_{o2})$$

$$R_{o2} = 1.632 \Omega$$

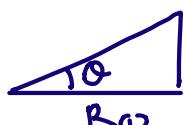

$$\tan\theta = \frac{X_{o2}}{R_{o2}}$$

$$\tan(50.586) = \frac{X_{o2}}{1.632}$$

$$X_{o2} = 1.9858 \Omega$$

[continue ...]

6 a)

$$\begin{aligned} R_{01} &= a^2 R_{02} \\ &= \left(\frac{1}{2}\right)^2 1.632 \\ &= 0.408 \cancel{\lambda} \end{aligned}$$

$$\begin{aligned} X_{01} &= a^2 X_{02} \\ &= \left(\frac{1}{2}\right)^2 (1.9858) \\ &= 0.496 \cancel{\lambda} \end{aligned}$$


b) $\eta = \frac{P_{out}}{P_{in}} \times 100\%$. Given 4kVA, $\frac{V_1}{V_2} = \frac{200}{400}$, $P_f = 0.8$

$$= \frac{P_{out}}{P_{out} + P_{loss}} \times 100\% \quad P_{loss} = 65 + 80$$

$$= \frac{4000 (0.8)}{4000 (0.8) + 145} \times 100\% \quad = 145$$

$$= 95.7\% \quad \cancel{H}$$

7

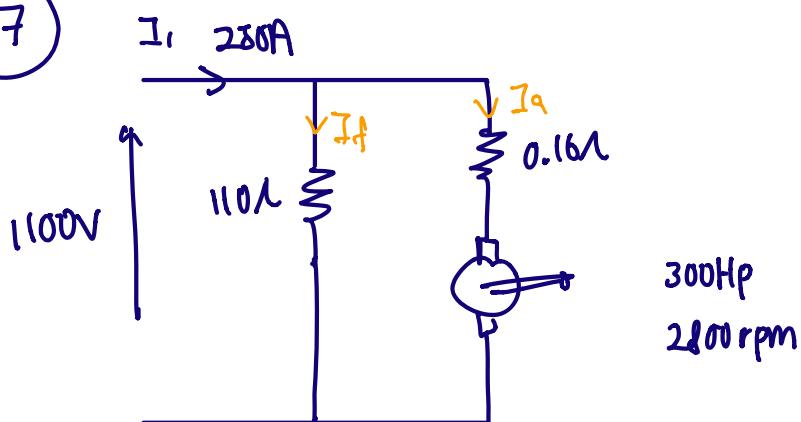

$$a) P = TW$$

$$300(745.7) = T \left(2800 \times \frac{2\pi}{60} \right)$$

$$T = 762.95 \text{ Nm}$$

$$I_r = I_f + I_a$$

$$E_a = 1100 - I_a(R_a)$$

$$250 = \frac{1100}{110} + I_a$$

$$= 1100 - 240(0.16)$$

$$I_a = 240 \text{ A}$$

$$= 1061.6 \text{ V}$$

$$E_a I_a = TW$$

$$1061.6(240) = T \left(2800 \times \frac{2\pi}{60} \right)$$

$$T = 868.931 \text{ Nm}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$


$$= \frac{300(745.7)}{1100(250)} \times 100\%$$

$$= 81.35\% \quad \cancel{H}$$

7 b) $P_{loss} = P_{dev} - P_{out}$

$$= 1061.6(240) - 300(745.7)$$

$$= \underline{31074W}$$

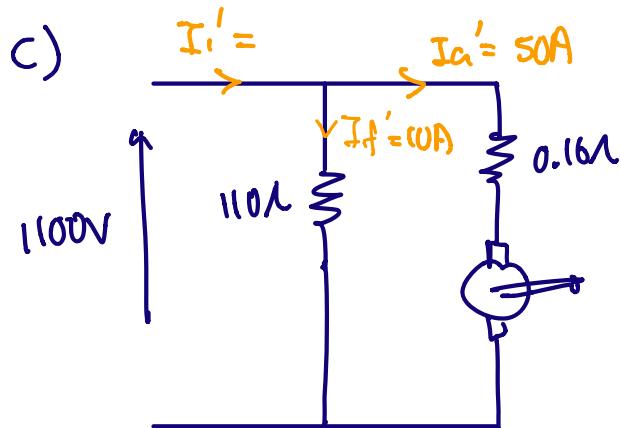

$$I_f' = \frac{1100}{110} = 10A$$

$$I_a' = 50$$

$$I_f \propto \phi$$

I_f constant so ϕ constant

$$E_a = K_a \phi \omega$$

$$\frac{E_a}{\omega} = k_a \phi$$

$$E_a' = 1100 - 50(0.16)$$

$$= 1092V$$

$$\frac{E_a}{\omega} = \frac{E_a'}{\omega'}$$

$$\frac{1061.6}{2800} = \frac{1092}{\omega'}$$

$$\omega' = 2880.18 \text{ rpm}$$

⑧ 15GWh per year

a) $\eta = \frac{P_{out}}{P_{in}} \times 100\%$.

$$21 = \frac{12.25 \times 10^6}{100(A)} \times 100\%$$

$$A = \underline{\underline{53030.3 \text{ m}^2}}$$

b) capacitor factor

$$= \frac{(15 \times 10^9)}{(12.25 \times 10^6)(365)(24)} \times 100\%$$

$$= \underline{\underline{14\%}}$$