

Mark Scheme for H61PWE Coursework 1

	Question in Lab sheet	Mark Available	Mark Awarded
Q1	What is the effective resistance of a) the ammeter and b) the voltmeter when connected in the circuit?	2	
Q2	Calculate the value of resistance you require for circuit 1 to have a supply current of 23mA.	1	
Q3	Measure the current and voltage in circuit 1 Do your measurements agree with your calculations (show calculation):	1	
Q4	calculate the power dissipated in the resistor	1	
Q5	Calculate the currents in R1, R2 and R3 and the voltages across each resistor	7	
Q6	Measure voltages and currents and compare with theory	1	
Q7	Calculate R4. Calculate $I_1 - I_4$ Evidence of using current divider rule Calculate voltages	10	
Q8	Demonstrate KVL Demonstrate relationship of $V_S$ to $V_{pq}$ , $V_{qr}$ , $V_{rs}$ using voltage divider	4	
Q9	From your measurements, state: 1) The potential of nodes P, Q, R and S 2) The voltage between nodes P and R 3) The voltage between nodes S and Q.	6	
Q10	Show that $V_{qr}$ can be calculated knowing the potentials at node Q and Node R.	1	
Q11	Figure 7 - Calculate the theoretical values for the voltages $V_{AB}$ $V_{BC}$ $V_{CD}$ and $V_{DE}$ . Show your working. Use these values to calculate $V_{EC}$	5	
Q12	What are the potentials at nodes A-E  Use these potentials to calculate the values of $V_{AB}$ and $V_{CD}$ and confirm your calculations from (Q11).	7	
Q13	Do the measured potentials match the theoretical values calculated in (Q12)?	2	
Q14	Do your measurements demonstrate the "voltage divider" rule?	1	
Q15	Change $R_{load}$ to 500k $\Omega$ and run the simulation. What happens to $V_{out}$ ?	1	
Q16	Change $R_{load}$ to 50k $\Omega$ and run the simulation. What happens to $V_{out}$ ?	2	
Q17	What conclusions can you draw about the potential divider rule?	2	
	Marks for presentation, organisation etc	6	
	<b>Total Mark</b>	<b>60</b>	